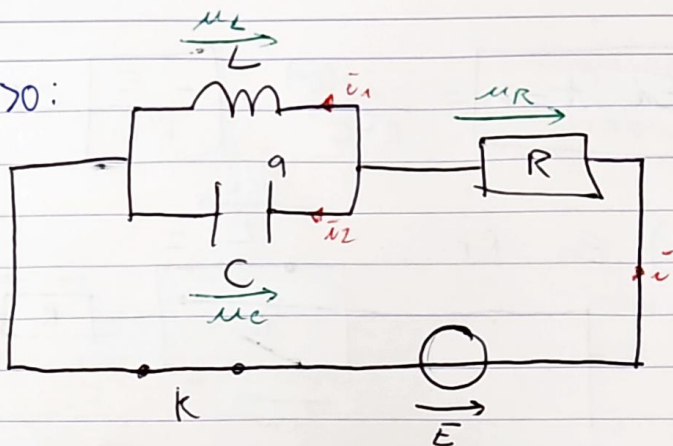


Exercice 6 : pour $t > 0$:

1) À $t=0^-$: C déchargé : $u_C(0^-) = 0 \Rightarrow C \equiv \text{---}$
 donc L court-circuité : $i_1(0^-) = 0$

À $t=0^+$: les discontinuités / tension aux bornes C : $u_C(0^+) = 0$
 courant aux bornes L : $i_1(0^+) = 0$
 dans

$$\text{LDM : } i = i_1 + i_2$$

$$\text{donc } i(0^+) = i_1(0^+) + i_2(0^+)$$

$$\Rightarrow i(0^+) = i_2(0^+)$$

$$\left. \begin{array}{l} q(0^+) = u_C(0^+) \times C \\ \Rightarrow q(0^+) = 0 \end{array} \right\}$$

$$\text{LDM : } E = u_R + u_C$$

$$\text{donc } E = u_R(0^+) + u_C(0^+)$$

$$\Rightarrow E = u_R(0^+)$$

$$\text{Loi d'Ohm (circuit récepteur) : } u_R(0^+) = R i(0^+)$$

$$\Rightarrow i(0^+) = \frac{E}{R}$$

$$\Rightarrow i_2(0^+) = \frac{E}{R}$$

$$\text{Loi d'Ohm (circuit récepteur) : } u_R = R i$$

LDM :

$$E - u_C = R i$$


$$\Rightarrow \frac{1}{R} (E - u_C) = i$$

$$\Rightarrow \frac{1}{R} \frac{d(E - u_C)}{dt} = \frac{di}{dt}$$

$$\Rightarrow -\frac{1}{R} \frac{du_C}{dt} = \frac{di}{dt}$$

$$\Rightarrow -\frac{1}{R} \frac{i_2}{C} = \frac{di}{dt}$$
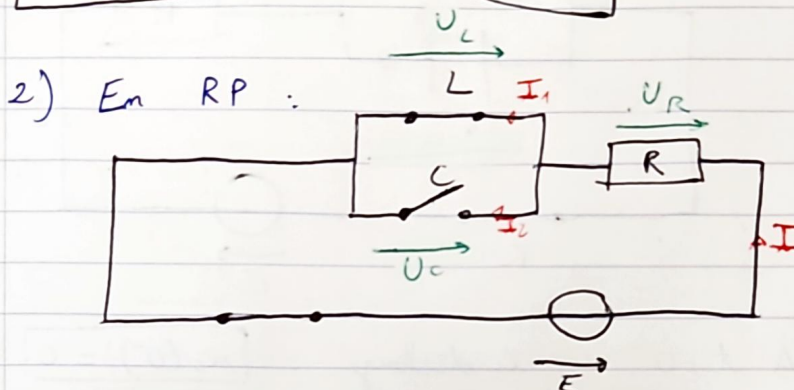
$$\left(\frac{di(t)}{dt} \right)_{t=0^+} = \frac{-\tilde{i}_2(0^+)}{R \cdot C} = \boxed{-\frac{E}{R^2 C}} < 0$$



$C \equiv \text{---} \text{---} \text{---}$ donc $\boxed{I_2 = 0}$

$L \equiv \text{---} \text{---} \text{---}$ donc $U_L = 0$

LDN: $I = I_1 + I_2 \Leftrightarrow I = I_1$

LDN: $E = U_R + U_L$
 $= U_R$

Loi d'Ohm (comme recept): $U_R = R I$

$\Leftrightarrow \boxed{I = \frac{E}{R} = I_1}$

$q_p = U_C \times C$ or $U_L = U_C = 0$
 $\Leftrightarrow \boxed{q_p = 0}$

$$\left(\frac{di(t)}{dt} \right)_{t=\infty} = \frac{-I_2}{RC} = \boxed{0}$$



4) LDM : $E = u_R + u_C$

$$E = u_R + u_L$$

LDN : $i = i_1 + i_2$

Loi d'Ohm (circuit récept.) : $u_R = R i$

Loi courant-tension (circuit récept.) : $i_2 = C \frac{du_C}{dt}$

$$u_L = L \frac{di_1}{dt}$$

$$E = u_R + u_L$$

$$\Rightarrow E = R i + L \frac{di_1}{dt}$$

$$\Rightarrow E = R i + L \frac{di}{dt} - L \frac{di_2}{dt}$$

$$\Rightarrow E = R i + L \frac{di}{dt} - LC \frac{d^2 u_C}{dt^2}$$

$$\Rightarrow E = R i + L \frac{di}{dt} - LC \frac{d^2 E - u_R}{dt^2}$$

$$\Rightarrow E = R i + L \frac{di}{dt} + LC \frac{d^2 u_R}{dt^2}$$

$$\Rightarrow E = R i + L \frac{di}{dt} + LCR \frac{d^2 i}{dt^2}$$

$$\Rightarrow \frac{E}{LCR} = \frac{d^2 i}{dt^2} + \frac{1}{RC} \frac{di}{dt} + \frac{1}{LC} i$$

$$\Rightarrow \boxed{\omega_0^2 \frac{E}{R} = \frac{d^2 i}{dt^2} + \frac{\omega_0}{Q} \frac{di}{dt} + \omega_0^2 i \quad \text{avec} \quad \omega_0 = \frac{1}{\sqrt{LC}}}$$

$$E = u_R + u_L$$

$$\Leftrightarrow E = Ri + L \frac{di_1}{dt}$$

$$\Leftrightarrow E = R(i_1 + i_2) + L \frac{di_1}{dt}$$

$$\Leftrightarrow E = Ri_1 + Ri_2 + L \frac{di_1}{dt}$$

$$\Leftrightarrow E = Ri_1 + RC \frac{du_C}{dt} + L \frac{di_1}{dt}$$

$$\Leftrightarrow E = Ri_1 + RC \frac{d(E - u_R)}{dt} + L \frac{di_1}{dt}$$

$$\Leftrightarrow E = Ri_1 + RC \frac{d(E - E + u_L)}{dt} + L \frac{di_1}{dt}$$

$$\Leftrightarrow E = Ri_1 + RCL \frac{d^2 i_1}{dt^2} + L \frac{di_1}{dt}$$

$$\Leftrightarrow \frac{E}{RLC} = \frac{d^2 i_1}{dt^2} + \frac{1}{RC} \frac{di_1}{dt} + \frac{1}{LC} i_1$$

$$\Leftrightarrow \omega_0^2 \frac{E}{R} = \frac{d^2 i_1}{dt^2} + \frac{\omega_0}{Q} \frac{di_1}{dt} + \omega_0^2 i_1 \quad \text{avec } \omega_0 = \frac{1}{\sqrt{LC}}$$